



EE3300 : Analog Circuits

Mini Project 3

EE19BTECH11041,
Srijith Reddy Pakala
Department of Electrical Engineering
IIT Hyderabad

December 11, 2021

Contents

| | | |
|----------|-----------------------------|-----------|
| 1 | Question 1 | 2 |
| 1.1 | Problem Statement | 2 |
| 1.2 | Spice Netlist | 3 |
| 1.3 | Plots | 13 |
| 2 | Question 2 | 16 |
| 2.1 | Problem Statement | 16 |
| 2.2 | Spice Netlist | 17 |
| 2.3 | Plots | 18 |

1 Question 1

1.1 Problem Statement

1. Design a two-stage opamp (miller-compensated) in 65 nm CMOS process with the following specifications:

- . • Supply voltage: 1.1 V.
- . • Input common-mode voltage: 0.55 V.
- . • Load capacitance: 10 pF.
- . • Unity gain bandwidth: 10 MHz.
- . • Phase-margin: 60 degrees.
- . • DC gain ≥ 40 dB
- . • Slew rate $\geq 10\text{V}/\mu\text{s}$.

Objective is to minimize power consumption while satisfying the above specifications.

Design should include biasing circuitry.

Submit hand calculations used to find:

- . • First and second stage transconductance.
- . • Miller cap and/or zero-nulling resistor.
- . • First and second stage bias-current.

Submit the netlist and the following frequency responses:

- . • Bode plot.
- . • Common-mode rejection ratio (CMRR).
- . • Power-supply rejection ratio (PSRR).

1.2 Spice Netlist

Bodeplot

```

M1 N003 Vn N004 N004 NMOS l=L w=W1 ad='2*65n*W1' as='2*65n*W1' pd='2*(2*65n+W1)'
ps='2*(2*65n+W1)' m=M
M2 N001 Vp N004 N004 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M
M3 VDD N003 N003 VDD PMOS l=L w=W3 ad='2*65n*W3' as='2*65n*W3' pd='2*(2*65n+W3)'
ps='2*(2*65n+W3)' m=M
M4 VDD N003 N001 VDD PMOS l=L w=W4 ad='2*65n*W4' as='2*65n*W4' pd='2*(2*65n+W4)'
ps='2*(2*65n+W4)' m=M
M5 N004 Vb VSS VSS NMOS l=L w=W5 ad='2*65n*W5' as='2*65n*W5' pd='2*(2*65n+W5)'
ps='2*(2*65n+W5)' m=M
M6 VDD N001 Out VDD PMOS l=L w=W6 ad='2*65n*W6' as='2*65n*W6' pd='2*(2*65n+W6)'
ps='2*(2*65n+W6)' m=M
M7 Out Vb VSS VSS NMOS l=L w=W7 ad='2*65n*W7' as='2*65n*W7' pd='2*(2*65n+W7)'
ps='2*(2*65n+W7)' m=M
Cc N002 Out 2.3p
M9 Vb Vb VSS VSS NMOS l=L w=W9 ad='2*65n*W9' as='2*65n*W9' pd='2*(2*65n+W9)'
ps='2*(2*65n+W9)' m=M
I1 VDD Vb 23u
CL Out 0 10p
V1 VDD 0 1.1
V2 0 VSS 1.1
vcm N006 0 0.55
vin N005 0 0 AC 1
E1 Vp N006 N005 0 0.5
E2 Vn N006 N005 0 -0.5
M8 N001 VDD N002 N002 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M
.model NMOS NMOS
.model PMOS PMOS
.lib standard.mos
.param L=1u M=1 W1=1.6u W2=1.6u W3=35u W4=35u W5=2.14u W6=160u W7=4u
W8=25u W9=2.14u
.include 65nm_NMOS_bulk.pm
.include 65nm_PMOS_bulk.pm
.ac dec 1000 1m 1G
.backanno
.end

```

CMRR

XX1 VDD N001 N003 Out VSS twostageopamp

V1 VDD 0 1.1

V2 0 VSS 1.1

R1 Out N001 1Meg

R2 N001 N002 1Meg

R3 N003 N002 1Meg

R4 0 N003 1Meg

V3 N002 0 0.55 AC 1

C1 Out 0 10p

* block symbol definitions

.subckt twostageopamp VDD Vn Vp Out VSS

M1 N003 Vn N004 N004 NMOS l=L w=W1 ad='2*65n*W1' as='2*65n*W1' pd='2*(2*65n+W1)'
ps='2*(2*65n+W1)' m=M

M2 N001 Vp N004 N004 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M

M3 VDD N003 N003 VDD PMOS l=L w=W3 ad='2*65n*W3' as='2*65n*W3' pd='2*(2*65n+W3)'
ps='2*(2*65n+W3)' m=M

M4 VDD N003 N001 VDD PMOS l=L w=W4 ad='2*65n*W4' as='2*65n*W4' pd='2*(2*65n+W4)'
ps='2*(2*65n+W4)' m=M

M5 N004 N005 VSS VSS NMOS l=L w=W5 ad='2*65n*W5' as='2*65n*W5' pd='2*(2*65n+W5)'
ps='2*(2*65n+W5)' m=M

M6 VDD N001 Out VDD PMOS l=L w=W6 ad='2*65n*W6' as='2*65n*W6' pd='2*(2*65n+W6)'
ps='2*(2*65n+W6)' m=M

M7 Out N005 VSS VSS NMOS l=L w=W7 ad='2*65n*W7' as='2*65n*W7' pd='2*(2*65n+W7)'
ps='2*(2*65n+W7)' m=M

Cc1 N002 Out 2.3p

M8 N005 N005 VSS VSS NMOS l=L w=W9 ad='2*65n*W9' as='2*65n*W9' pd='2*(2*65n+W9)'
ps='2*(2*65n+W9)' m=M

I1 VDD N005 23μ

M9 N001 VDD N002 N002 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M

.param L=1u M=1 W1=1.6u W2=1.6u W3=35u W4=35u W5=2.14u W6=160u W7=4u
W8=25u W9=2.14u

.include 65nm_NMOS_bulk.pm

.include 65nm_P MOS_bulk.pm

.ends twostageopamp

.model NMOS NMOS

.model PMOS PMOS

.lib C:standard.mos

.ac dec 1000 1m 1G

.backanno

.end

PSRR

XX1 VDD Out N001 Out VSS twostageopamp

V1 VDD 0 1.1 AC 1

V2 0 VSS 1.1

V3 N001 0 0.55

C1 Out 0 10p

* block symbol definitions

.subckt twostageopamp VDD Vn Vp Out VSS

M1 N003 Vn N004 N004 NMOS l=L w=W1 ad='2*65n*W1' as='2*65n*W1' pd='2*(2*65n+W1)'
ps='2*(2*65n+W1)' m=M

M2 N001 Vp N004 N004 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M

M3 VDD N003 N003 VDD PMOS l=L w=W3 ad='2*65n*W3' as='2*65n*W3' pd='2*(2*65n+W3)'
ps='2*(2*65n+W3)' m=M

M4 VDD N003 N001 VDD PMOS l=L w=W4 ad='2*65n*W4' as='2*65n*W4' pd='2*(2*65n+W4)'
ps='2*(2*65n+W4)' m=M

M5 N004 N005 VSS VSS NMOS l=L w=W5 ad='2*65n*W5' as='2*65n*W5' pd='2*(2*65n+W5)'
ps='2*(2*65n+W5)' m=M

M6 VDD N001 Out VDD PMOS l=L w=W6 ad='2*65n*W6' as='2*65n*W6' pd='2*(2*65n+W6)'
ps='2*(2*65n+W6)' m=M

M7 Out N005 VSS VSS NMOS l=L w=W7 ad='2*65n*W7' as='2*65n*W7' pd='2*(2*65n+W7)'
ps='2*(2*65n+W7)' m=M

Cc1 N002 Out 2.3p

M8 N005 N005 VSS VSS NMOS l=L w=W9 ad='2*65n*W9' as='2*65n*W9' pd='2*(2*65n+W9)'
ps='2*(2*65n+W9)' m=M

I1 VDD N005 23μ

M9 N001 VDD N002 N002 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M

.param L=1u M=1 W1=1.6u W2=1.6u W3=35u W4=35u W5=2.14u W6=160u W7=4u
W8=25u W9=2.14u

.include 65nm_NMOS_bulk.pm

.include 65nm_PMOS_bulk.pm

.ends twostageopamp

.model NMOS NMOS

.model PMOS PMOS


.lib C:standard.mos

.ac dec 1000 1m 1G

.backanno

.end

Two stage - opamp (Miller Compensated)

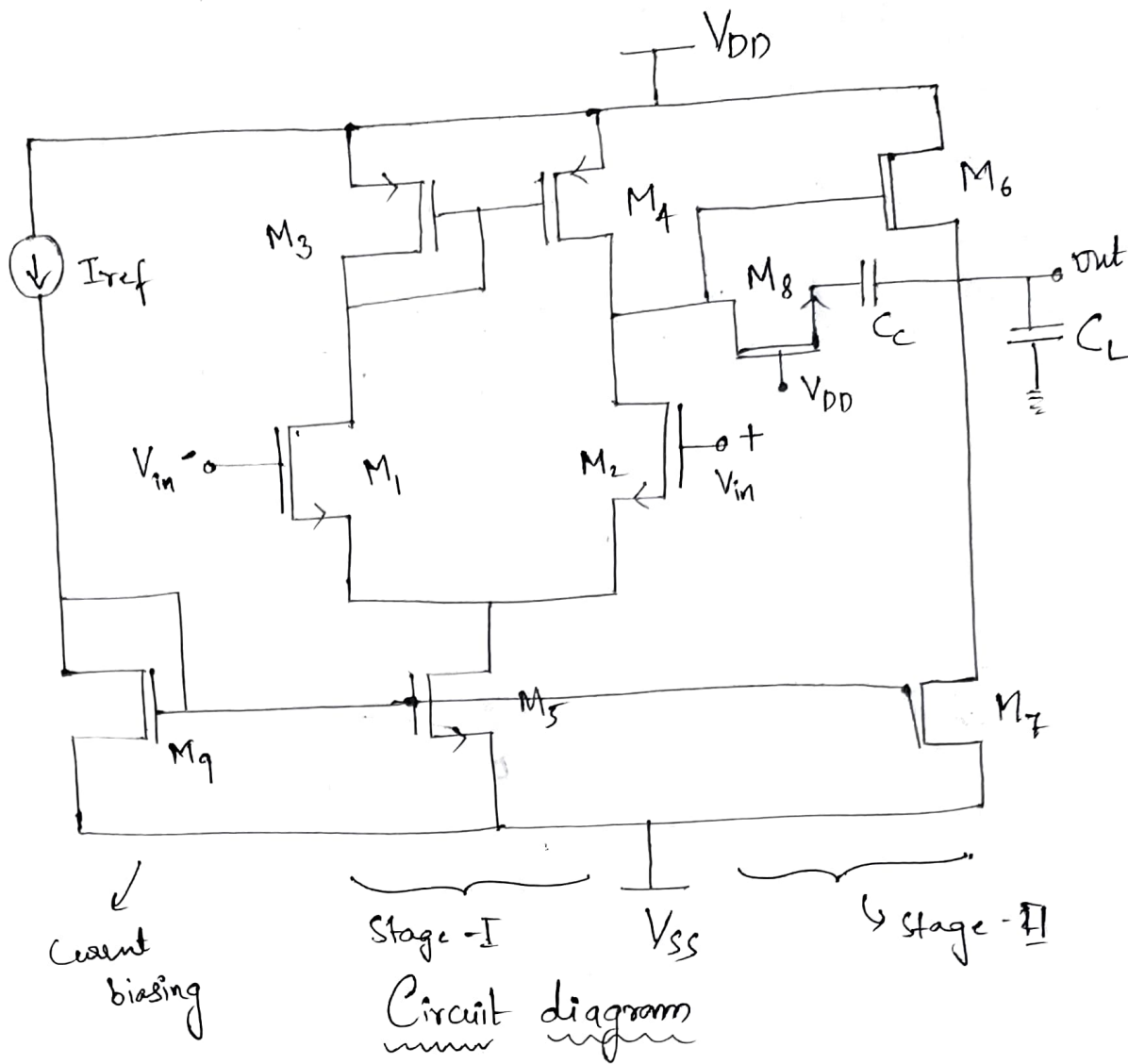

$$A(s) = \frac{A_0 \left(1 - \frac{s}{z}\right)}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right)}$$

$$Z = \frac{g_{m6}}{C_c}$$

$$p_1 = \frac{GB}{A_{V(0)}} \Rightarrow \text{Since } 20 \log(A) = 20 \log\left(\frac{GB}{p_1}\right)$$

$$p_2 \approx \frac{g_{m2}}{C_L}$$

$$PM = 180^\circ - \tan^{-1}\left(\frac{\omega}{|P_1|}\right) - \tan^{-1}\left(\frac{\omega}{|P_2|}\right) - \tan^{-1}\left(\frac{\omega}{|Z|}\right) = 60^\circ$$

$$\omega = G_B, \quad Z > G_B \Rightarrow Z = 10 G_B$$

$$\Rightarrow 180^\circ - \tan^{-1}(A_V(0)) - \tan^{-1}\left(\frac{G_B}{|P_2|}\right) - \tan^{-1}(0.1) = 60^\circ$$

$$= 90^\circ$$

$$\Rightarrow |P_2| \geq 2.215 G_B$$

$$|Z| \geq 10 G_B \Rightarrow \frac{g_{m6}}{C_c} \geq 10 \frac{g_{m1}}{C_c}$$

$$\Rightarrow g_{m6} \geq 10 g_{m1}$$

$$|P_2| \geq 2.215 G_B$$

$$\Rightarrow \frac{g_{m6}}{C_L} \geq \frac{g_{m1}}{C_c} \times 2.215$$

$$\Rightarrow \boxed{C_c \geq 0.2215 C_L}$$

$$C_L = 10 \text{ pF} \Rightarrow C_c \geq 2.215 \text{ pF}, \quad \boxed{C_c = 2.3 \text{ pF}}$$

$$\text{Given} \quad \text{slew rate} = \frac{I_S}{C_c} > 10 \text{ V}/\mu\text{s}$$

$$\Rightarrow I_S \geq 2.3 \times 10^{-2} \times 10 \times 10^6$$

$$\Rightarrow I_{S \text{ min}} = 23 \mu\text{A}$$

Now we know $g_{m6} = 10 g_{m1}$

$$A_0 = \frac{2 g_{m1} g_{m6}}{P_5 P_6 (\lambda_2 + \lambda_4) (\lambda_6 + \lambda_7)}$$

From Mini-project-1

$$K_n' = 569 \mu \text{ (short)}$$

$$\lambda_n = 0.87 \text{ C}$$

$$K_n' = 541 \mu \text{ (long)}$$

$$K_p' = 184 \mu \text{ (short)}$$

$$\lambda_p = 1.14$$

$$K_p' = 491 \mu \text{ (long)}$$

$$A_0 \geq 40 \text{ dB} \Rightarrow \frac{2 g_{m1} \times 10 g_{m1}}{23 \times 10^{-6} \times 4 \times \frac{g_{m6}^2}{2 K_p' \left(\frac{W}{L} \right)_6}} > 100$$

$$\Rightarrow \left(\frac{W}{L} \right)_6 > 125$$

To find g_{m1}

$$g_{m1} = GBC_c = 2 \times \pi \times 10 \times 10^6 \times 2.3 \times 10^{-12} = 144.5 \mu\Omega^{-1}$$

$$g_{m6} = 10 g_{m1} = 1.44 \text{ m}\Omega^{-1}$$

Input common mode range

$$V_{SS} + V_{DSAT3} + V_{DSAT1} + V_{TN} < V_{icm} < V_{DD} - V_{DSAT3} - V_{TP} + V_{TN}$$

$$\textcircled{8} \quad V_{icm} = 0.55 \text{ V}, \quad V_{DSAT} = 0.2 \text{ V}, \quad |V_T| = 0.4 \text{ V}$$

$$\Rightarrow 0.55 > V_{SS} + 0.8$$

$$\Rightarrow V_{SS} < -0.25$$

$$\text{Let's take } V_{SS} = -V_{DD} = -1.1 \text{ V}$$

$$0.55 < 1.1 - 0.2 - 0.4 + 0.4 \rightarrow \text{verified.}$$

$$\left(\frac{W}{L}\right)_{3,4} > \frac{I_S}{K_p [V_{DSAT3}]^2}$$

$$\Rightarrow \boxed{\left(\frac{W}{L}\right)_{3,4} > 1.6}$$

Now $S_{1,2}$

$$\left(\frac{W}{L}\right)_{1,2} = \frac{g_{m1}^2}{2K_n' I_1} = \frac{(144 \times 10^{-6})^2}{2 \times 569 \times 10^{-6} \times \frac{23}{2} \times 10^{-6}}$$

$$\left(\frac{W}{L}\right)_{1,2} = 1.6$$

Similar to $S_{3,4}$

$$V_{Dsat5} = 0.2$$

$$S_5 \geq \frac{2I_5}{K_n'(V_{Dsat5})^2} = 2$$

$$\Rightarrow \left(\frac{W}{L}\right)_5 \geq 2$$

From DC balance equations

~~(Scribbled out text)~~

$$V_{S06} = V_{S04}$$

$$S_6 = \frac{g_{m6}}{g_{m4}} S_4$$

$$\Rightarrow \left(\frac{W}{L}\right)_6 = 22.15 \sqrt{\left(\frac{W}{L}\right)_4} > 125$$

$$\Rightarrow \left(\frac{W}{L}\right)_4 > 31$$

Therefore let's take $\left(\frac{W}{L}\right)_{3A} = 35$

$$\Rightarrow \left(\frac{W}{L}\right)_6 = 131$$

$$I_6 = \frac{(g_{m6})^2}{2K_p \times \left(\frac{W}{L}\right)_6} = 43 \mu A$$

$$\left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_5 \times \frac{I_6}{I_5} \geq 3.74$$

$$\text{Let's take } S_7 = 4 \Rightarrow S_5 = 2.14$$

Now Nulling Resistor

for Z to on top of P_2

$$R_z = \frac{1}{g_{m6}} \left(\frac{C_L + C_c}{C_c} \right), \text{ Since } R_z \text{ is realised using NMOS}$$

$$\Rightarrow \left(\frac{W}{L}\right)_8 = \frac{\left(\frac{W}{L}\right)_6}{1 + \frac{C_L}{C_c}} = 25$$

Let Recheck the gain:

$$A_0 = \frac{2g_{m1}g_{m6}}{I_6(\lambda_6 + \lambda_7)(I_5)(\lambda_2 + \lambda_4)}$$
$$= \frac{2 \times 10 \times (144 \times 10^{-6})^2}{43 \times 10^{-6} \times 4 \times 23 \times 10^{-6}} \approx 104$$

Final Sizings

$$S_{1,2} = 1.6, \quad S_{3,4} = 35, \quad S_5 = 2.14, \quad S_6 = 131$$

$$S_7 = 4, \quad S_8 = 25$$


Sanity check ✓

For DC balance

$$\frac{S_6}{S_4} = \frac{2S_7}{S_5} = \frac{131}{35} = 2 \times \frac{4}{2.14} \quad (\text{verified})$$

1.3 Plots


Bodeplot

 


Bode plot

- We can see that the device satisfies all specified design requirements from the plot.

Common-mode rejection ratio (CMRR)

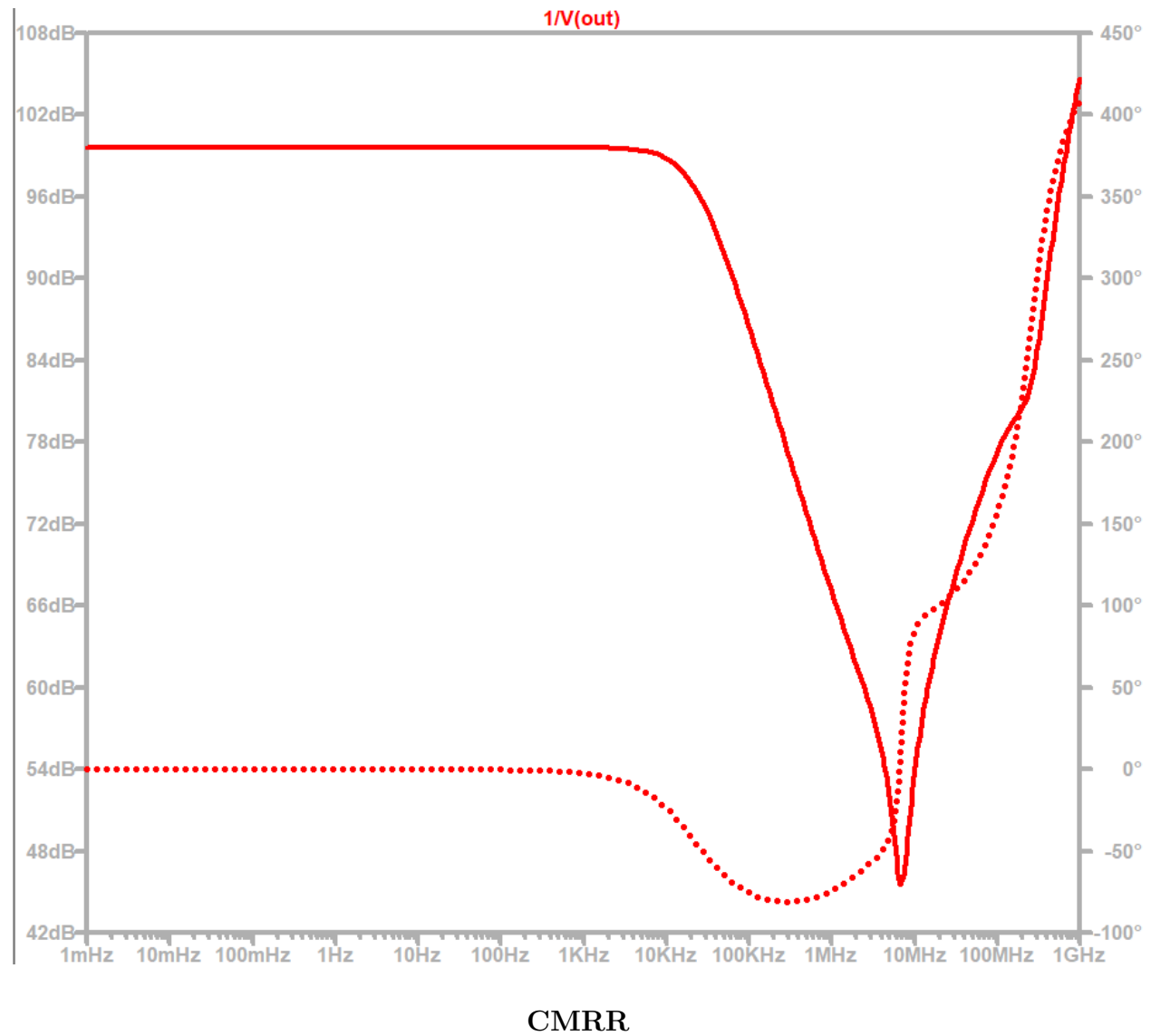

Power-supply rejection ratio (PSRR)

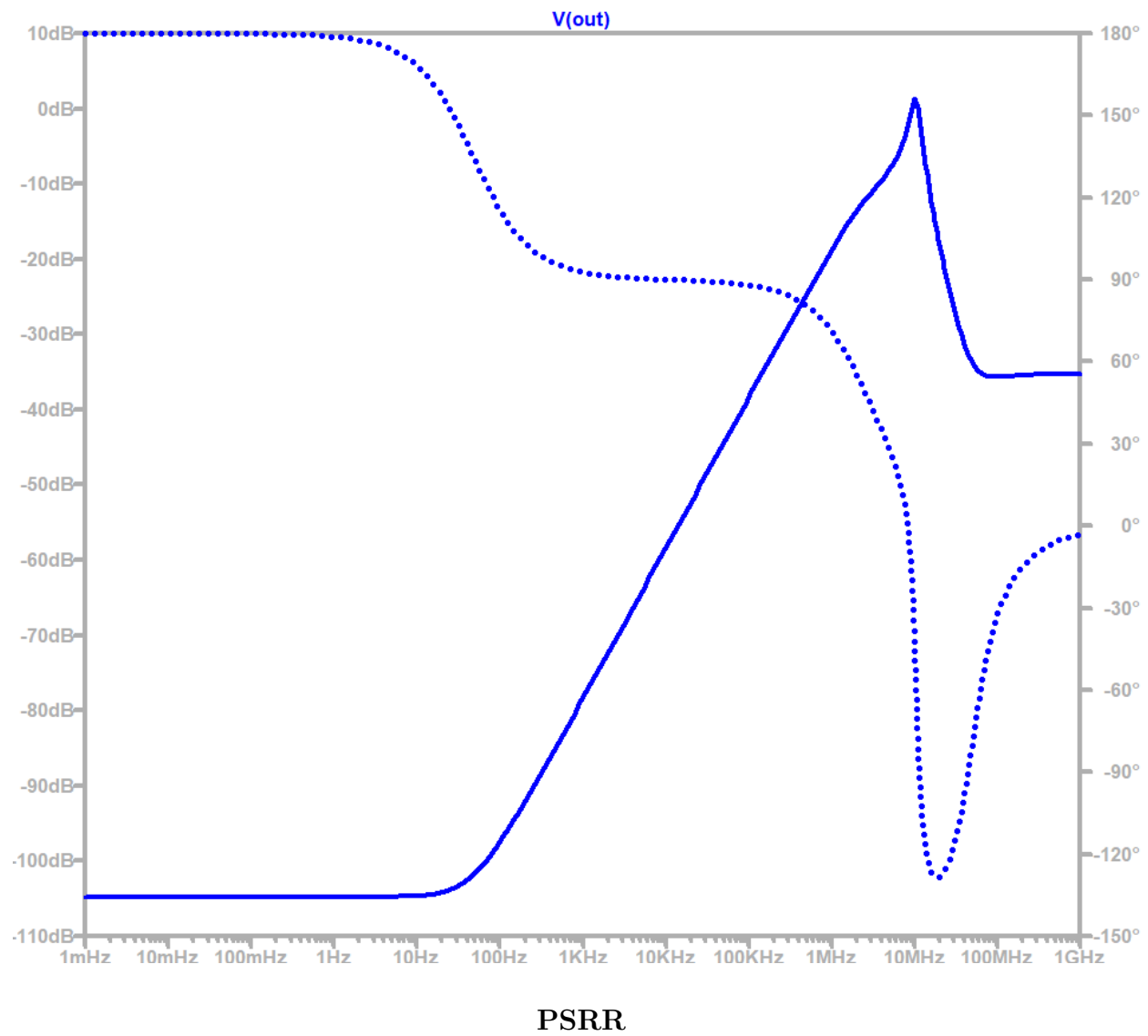

2 Question 2

2.1 Problem Statement

2. Connect the above op-amp in unity-gain feedback and submit the following plots:

- . • Step-response when the output starts slewing for both positive and negative steps.
- . • Output vs input when input DC voltage is varied from 0 V to supply voltage.
- . • Output spectrum when $(0.1 \sin 2\pi 1000t)$ V is applied at the input. Also calculate the total harmonic distortion (THD).

2.2 Spice Netlist

```


XX1 VDD Out N001 Out VSS twostageopamp
V1 VDD 0 1.1
V2 0 VSS 1.1
V3 N001 0 SINE(0 0.1 1k)
C1 Out 0 10p

* block symbol definitions
.subckt twostageopamp VDD Vn Vp Out VSS
M1 N003 Vn N004 N004 NMOS l=L w=W1 ad='2*65n*W1' as='2*65n*W1' pd='2*(2*65n+W1)'
ps='2*(2*65n+W1)' m=M
M2 N001 Vp N004 N004 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M
M3 VDD N003 N003 VDD PMOS l=L w=W3 ad='2*65n*W3' as='2*65n*W3' pd='2*(2*65n+W3)'
ps='2*(2*65n+W3)' m=M
M4 VDD N003 N001 VDD PMOS l=L w=W4 ad='2*65n*W4' as='2*65n*W4' pd='2*(2*65n+W4)'
ps='2*(2*65n+W4)' m=M
M5 N004 N005 VSS VSS NMOS l=L w=W5 ad='2*65n*W5' as='2*65n*W5' pd='2*(2*65n+W5)'
ps='2*(2*65n+W5)' m=M
M6 VDD N001 Out VDD PMOS l=L w=W6 ad='2*65n*W6' as='2*65n*W6' pd='2*(2*65n+W6)'
ps='2*(2*65n+W6)' m=M
M7 Out N005 VSS VSS NMOS l=L w=W7 ad='2*65n*W7' as='2*65n*W7' pd='2*(2*65n+W7)'
ps='2*(2*65n+W7)' m=M
Cc1 N002 Out 2.3p
M8 N005 N005 VSS VSS NMOS l=L w=W9 ad='2*65n*W9' as='2*65n*W9' pd='2*(2*65n+W9)'
ps='2*(2*65n+W9)' m=M
I1 VDD N005 23μ
M9 N001 VDD N002 N002 NMOS l=L w=W2 ad='2*65n*W2' as='2*65n*W2' pd='2*(2*65n+W2)'
ps='2*(2*65n+W2)' m=M
.param L=1u M=1 W1=1.6u W2=1.6u W3=35u W4=35u W5=2.14u W6=160u W7=4u
W8=25u W9=2.14u
.include 65nm_NMOS_bulk.pm
.include 65nm_PMOS_bulk.pm
.ends twostageopamp
.model NMOS NMOS
.model PMOS PMOS
.lib C:standard.mos
.tran 4m
.four 1kHz V(out)
.backanno
.end

```


2.3 Plots

Step Response

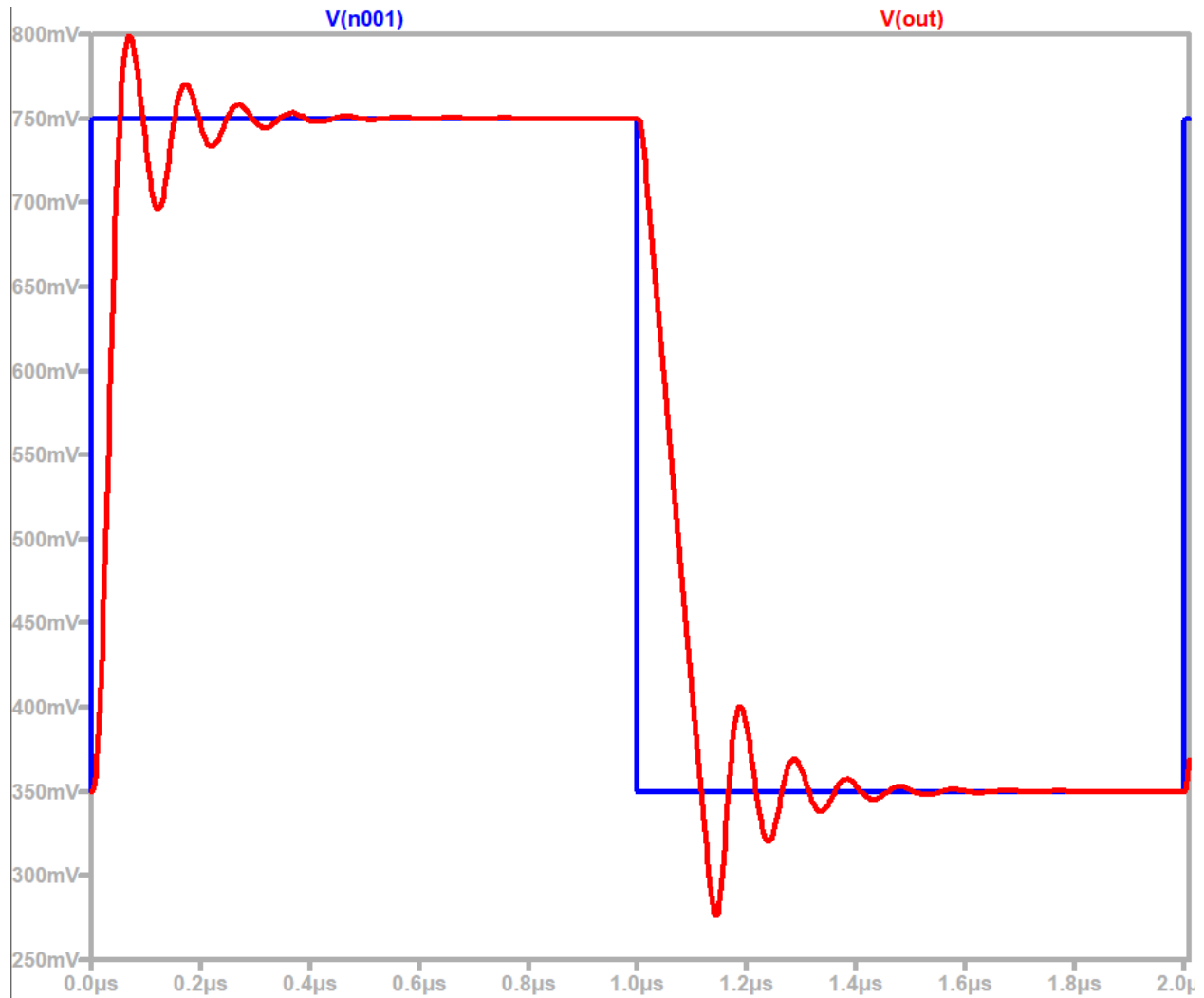

Output Response for pulse


Positive Step

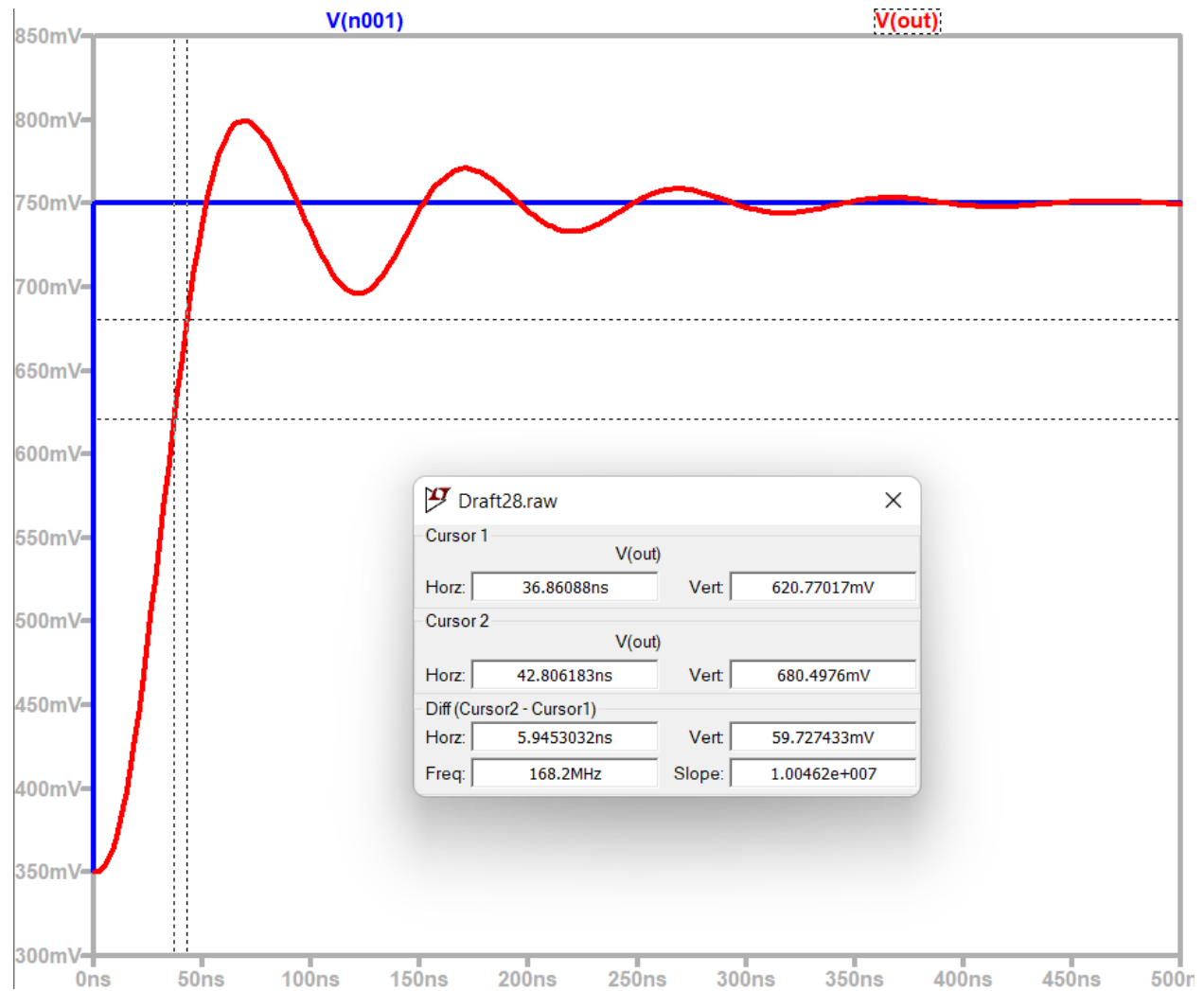

Positive Step Response

- Positive slew rate is $10.04 \text{ V}/\mu\text{s}$.


Negative Step

 


Negative Step Response

- Negative slew rate is $-3.65 \text{ V}/\mu\text{s}$.

Input Dc sweep Response

 

 Output spectrum when $V_{in} = (0.1 \sin 2\pi 1000t) \text{ V}$



- The total harmonic distortion (THD) is 0.111232%.

Thank
you