



Analog Circuits(EE3300)

Simulation Exercise 1

EE19BTECH11041,
Srijith Reddy Pakala
Department of Electrical Engineering
IIT Hyderabad

October 20, 2021

Contents

1	Problem statement	2
2	Hand Calculation	2
3	Schematic	7
4	Output	8
4.1	Output FFT For $V_{in} = 1\text{mV}$:	8
4.2	Output FFT For $V_{in} = 50\text{mV}$:	9
5	Frequency Response	10
6	DC power consumed by the amplifier.	10

1 Problem statement

1. Design an amplifier with biasing to meet the following specifications:

- Gain: 20 dB
- Source resistance: 1 k Ω
- Load resistance: 50 Ω
- Frequency: 1kHz

(Given: One voltage source of 1.1V and current source of 10 μ A.)(Given: One voltage source of 1.1V and current source of 10 μ A.)

Objective is to meet the above specifications while maximizing the signal swing. You can cascade multiple stages if needed.

Submit the following:

- Hand calculation for choosing the device size and biasing elements. Use the square-law model extracted in the previous exercise. Final values can be changed based on simulation.
- Schematic screenshot and Final element values.
- Total harmonic distortion (THD) measures linearity of a system,

$$THD = \frac{\sqrt{V_2^2 + V_3^2 + \dots + V_n^2}}{V_1} \quad (1)$$

where, V_k is the rms value of kth harmonic.

Calculate output voltage THD (in %) using LTspice for input amplitude of 1mV and 50 mV. Attach output FFT plots also.


- Frequency response from 10 Hz to 100 kHz.
- DC power consumed by the amplifier.
- Upload LTspice schematic as a separate file.

2 Hand Calculation

Hand Calculation



Single Cascade Circuit Block:

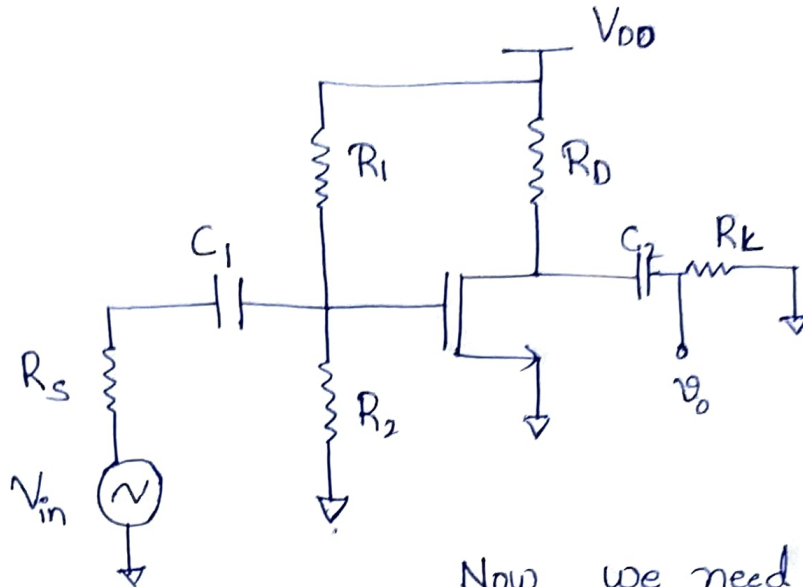

Now we need a total gain of 20dB


$$\Rightarrow \boxed{\frac{V_{o, \text{final}}}{V_{in}} = 10}$$

Here we are cascading so

Let's say gain in first cascade is K_1

$$\Rightarrow g_m (R_L // R_D) = K_1$$

Swing

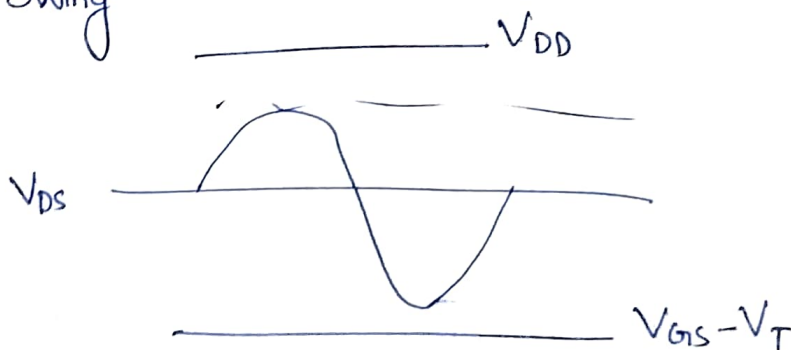

To maximize swing V_{DS} should be mid value of V_{DD} and $V_{GS} - V_T$.

$$V_{DS} = \frac{V_{DD} + V_{GS} - V_T}{2}$$

$$V_{DS} = V_{DD} - I_{DS} R_D$$

$$I_{DS} = \frac{g_m (V_{GS} - V_T)}{2}$$

$$\Rightarrow V_{DD} - \frac{g_m R_D}{2} (V_{GS} - V_T) = \frac{V_{DD}}{2} + \frac{V_{GS} - V_T}{2}$$

$$\Rightarrow (1 + g_m R_D) (V_{GS} - V_T) = V_{DD}$$

$$\Rightarrow (V_{GS} - V_T) = V_x = \frac{V_{DD}}{1 + g_m R_D}$$

$$V_{DS} = \frac{V_{DD} \left\{ \frac{2 + g_m R_D}{1 + g_m R_D} \right\}}{2}, \text{ But } g_m R_D \gg 1,$$

$$g_m R_D = 2 \times K = 2$$

$$V_{DS} \approx \frac{V_{DD}}{2} \approx \frac{1.1}{2} = 0.55V$$

$$V_{GS} = V_T + \frac{V_{DD}}{1 + g_m R_D} \approx \text{around } 0.55$$

To calculate $\frac{W}{L}$, let's take $V_{GS} = 0.55$, $R_D = R_L = 50$



$$\Rightarrow g_m = \frac{1 \text{ to } 10}{(R_D // R_L)} = \text{gain is in } 1 \text{ to } 10 \text{ because of cascade}$$

let's say 3.1

$$\Rightarrow g_m = \frac{3}{25}$$

$$\Rightarrow \beta \frac{W}{L} (V_{GS} - V_T) = \frac{3}{25} \quad (\beta = 560 \mu)$$

$$\Rightarrow \frac{W}{L} (560) \times 10^{-6} \times 0.15 = \frac{3}{25}$$

$$\Rightarrow \boxed{\frac{W}{L} \approx 1400}$$

Now from these calculation ranges and simulation values we will eventually get a gain of 10 after using some cascade.

Note:

* I haven't used current source anywhere.

* To maximize swing the last Block of cascade should have highest gain.

Now capacitances

$$\Rightarrow \frac{1}{\omega R} \ll C$$

$$\Rightarrow C_1 \gg \frac{1}{(2\pi \times 10^3) R}$$

$$\boxed{\omega = 2\pi \times 10^3}$$


$$\Rightarrow C_1 \gg \frac{1}{\omega (R_D // R_2 + R_S)}$$

$$\Rightarrow C_2 \gg \frac{1}{\omega (R_D // R_L)}$$

$$R_D // R_2 \gg R_S$$

Using this we can calculate and use capacitors.

3 Schematic

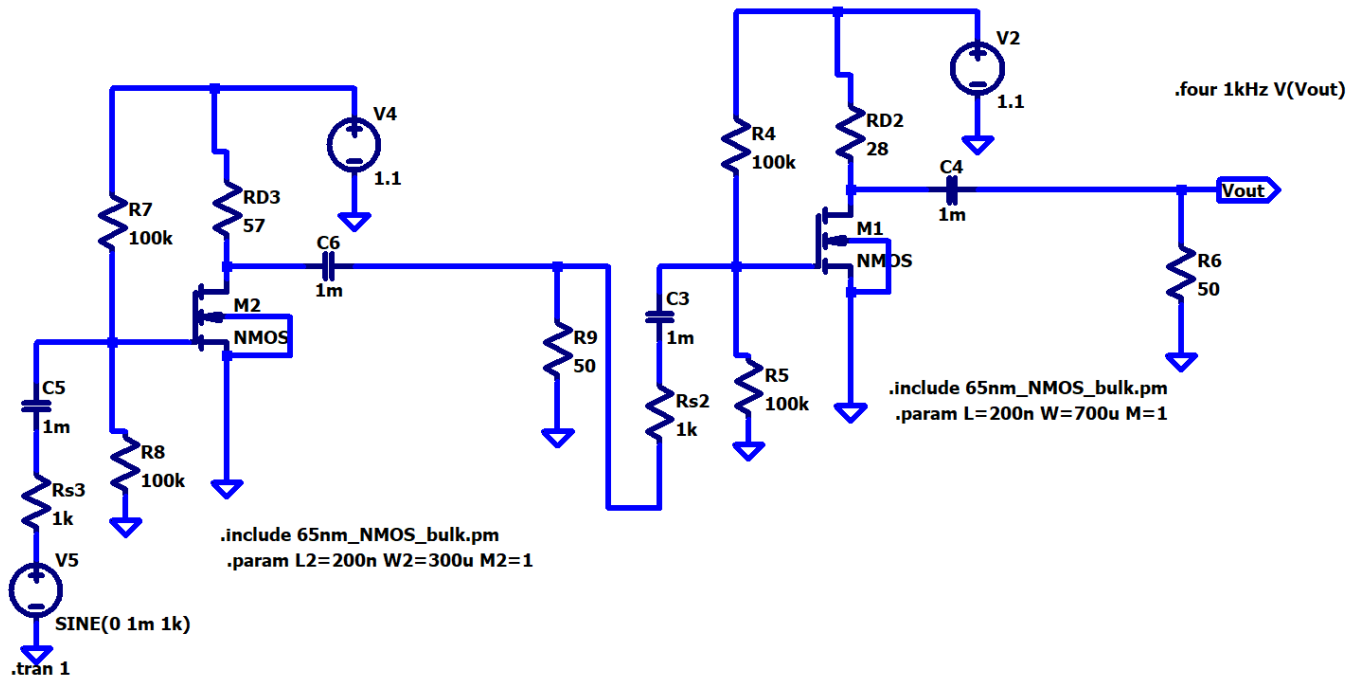

Amplifier Circuit Schematic




Cascade blocks

- The Gain of the first block is 2.7 and the second block is 3.7.
- The total gain is 10 i.e.

$$\frac{V_o}{V_{in}} = 10. \quad (2)$$

4 Output

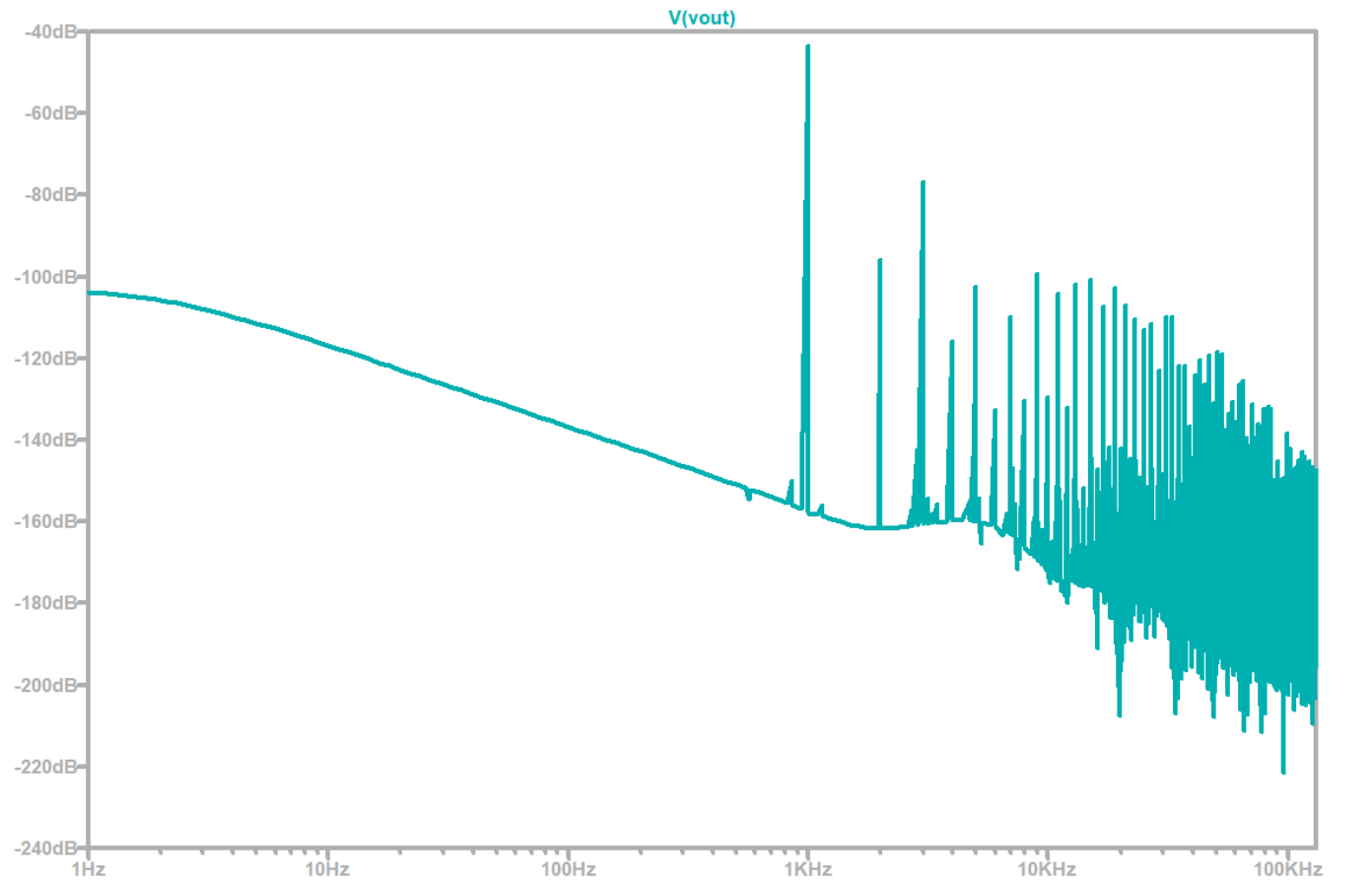
4.1 Output FFT For $V_{in} = 1\text{mV}$:



V_o FFT for $V_{in} = 1\text{mV}$

- Total Harmonic Distortion: 2.134221%.

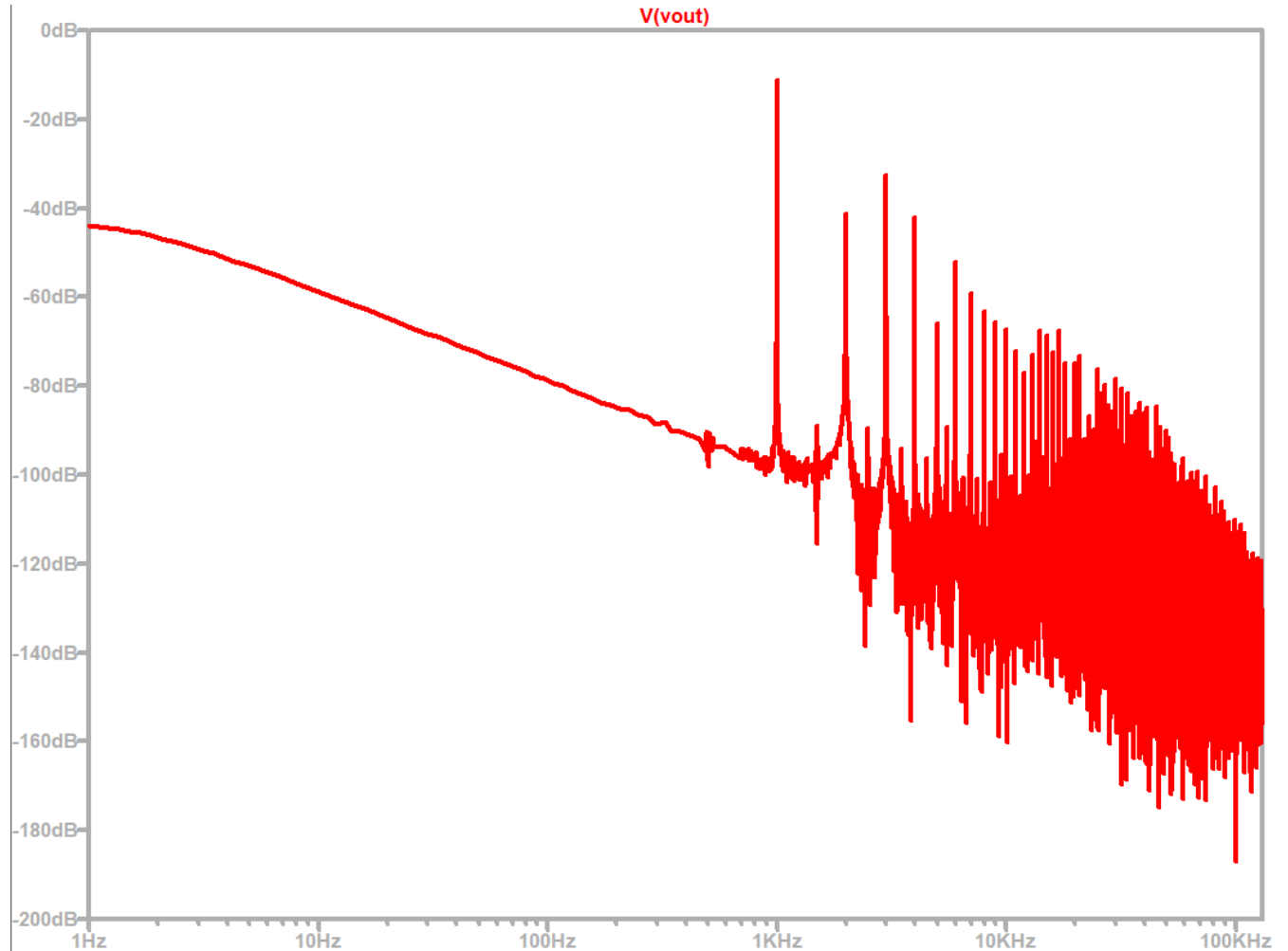
4.2 Output FFT For $V_{in} = 50\text{mV}$:



V_o FFT for $V_{in} = 50\text{mV}$

- Total Harmonic Distortion: 9.584068%.
- Here the Output gain was 7.2 because in simulation the swing limit was exceeded.

5 Frequency Response

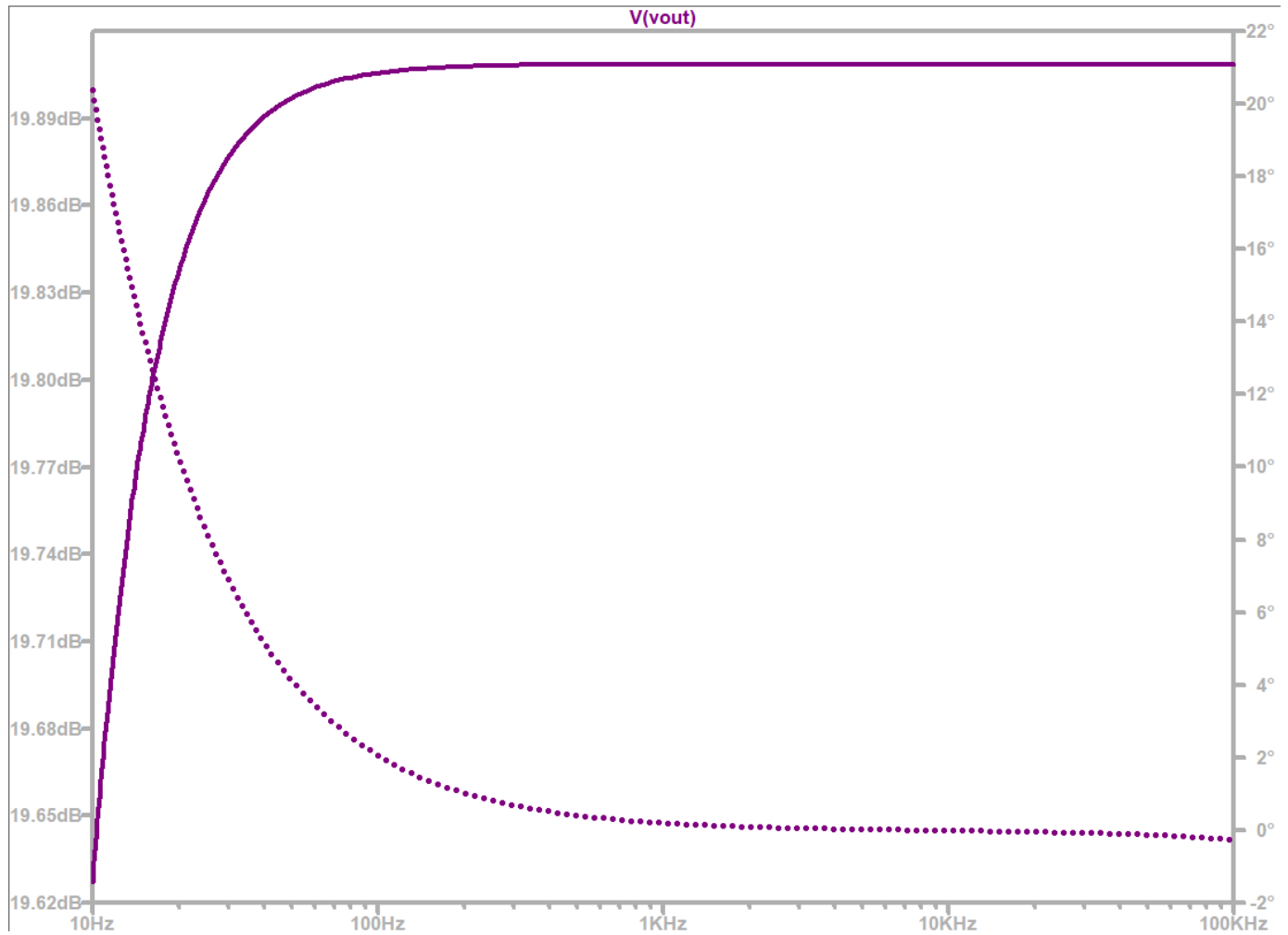

Frequency Response

6 DC power consumed by the amplifier.

The power for source is the DC power.

Refer to the schematic for component labels.

$$P_{DC} = V_{DD}(I(Rd3) + I(Rd2) + I(R7) + I(R4)) \quad (3)$$

- Here $I(Rd2) = 18.0271 \text{ mA}$, $I(Rd3) = 8.98041 \text{ mA}$, $I(R4) = 5.7543 \mu\text{A}$, $I(R7) = 5.62947 \mu\text{A}$.
- DC power is 29.7 mWatt.

Thank
you